

**BECC 0800: ELECTRONICS LAB-I**

**Semester I**

**L–T–P: 0–0–2**

**Credits: 01**

**List of Experiments**

1. Identification of various electronics, electrical components and study of measuring instruments and sources used in electronic circuits.  
(i) Multi-meters    (ii) CRO    (iii) Function Generator    (iv) DC Supply
2. To determine the V-I characteristics of a semi-conductor diode.
3. To study the working of a Half-Wave & Full Wave (Bridge type) rectifier.
4. To study application of diode as clipper circuit and clamper circuit.
5. To study Zener diode as voltage regulator
6. To study V-I characteristic of CE configuration of BJT.
7. To study V-I characteristic of JFET.
8. To study V-I characteristic of MOSFET.
9. To verify characteristics of op-Amp and realization of Op-Amp as adder & subtractor.
10. To study various logic gates such as OR, AND, NOT, NAND, NOR.
11. **Minor project based on experiments performed:**  
Realization of regulated power supply and its applications.

## INDEX

Name of student.....Class/ Batch..... Roll No. ....

Course/Branch..... Session..... Semester.....

Name of subject..... Subject Code.....

S. No.	Experiment	Date of Perform	Date of Submission	Grading scale(10)	Signature
1					
2					
3					
4					
5					
6					
7					
8					
9					
10					

**Overall Grading Average (10)=**

**Signature of Evaluator**

## **EXPERIMENT No.1**


**OBJECTIVE:** Identification of various electronics, electrical components and study of measuring instruments and sources used in electronic circuits.

(i) CRO (ii) Function Generator (iii) Multi-meter (iv) DC Supply

**APPARATUS & MATERIAL REQUIRED:-** Cathode-ray Oscilloscope, Function Generator, BNC to BNC co-axial cable, CRO Probes, multi-meter and dc power supply .

### **THEORY:**

**1. Cathode-Ray Oscilloscope:** The cathode-ray oscilloscope (CRO) is a common laboratory instrument that provides accurate time and amplitude measurements of voltage signals over a wide range of frequencies. Its reliability, stability, and ease of operation make it suitable as a general purpose laboratory instrument. The heart of the CRO is a cathode-ray tube shown schematically in Fig. 1.

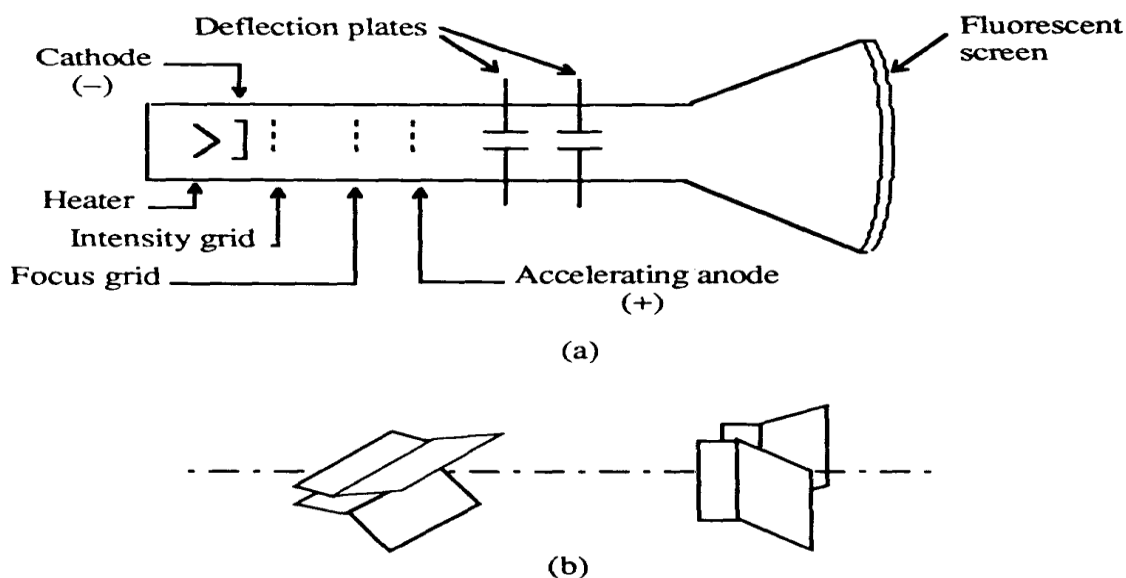

**Figure 1. Cathode-ray tube: (a) schematic, (b) detail of the deflection plates.**

The cathode ray is a beam of electrons which are emitted by the heated cathode (negative electrode) and accelerated toward the fluorescent screen. The assembly of the cathode, intensity grid, focus grid, and accelerating anode (positive electrode) is called an *electron gun*. Its purpose is to generate the electron beam and control its intensity and focus. Between the electron gun and the fluorescent screen, there are two pair of metal plates - one oriented to provide horizontal deflection of the beam and one pair oriented to give vertical deflection to the beam. These plates are thus referred to as the *horizontal* and *vertical deflection plates*. The combination of these two deflections allows the beam to reach any portion of the fluorescent screen. Wherever the electron beam hits the screen, the *phosphor* is excited and light is emitted from that point. This conversion of electron energy into light allows us to write with points or lines of light on an otherwise darkened screen.

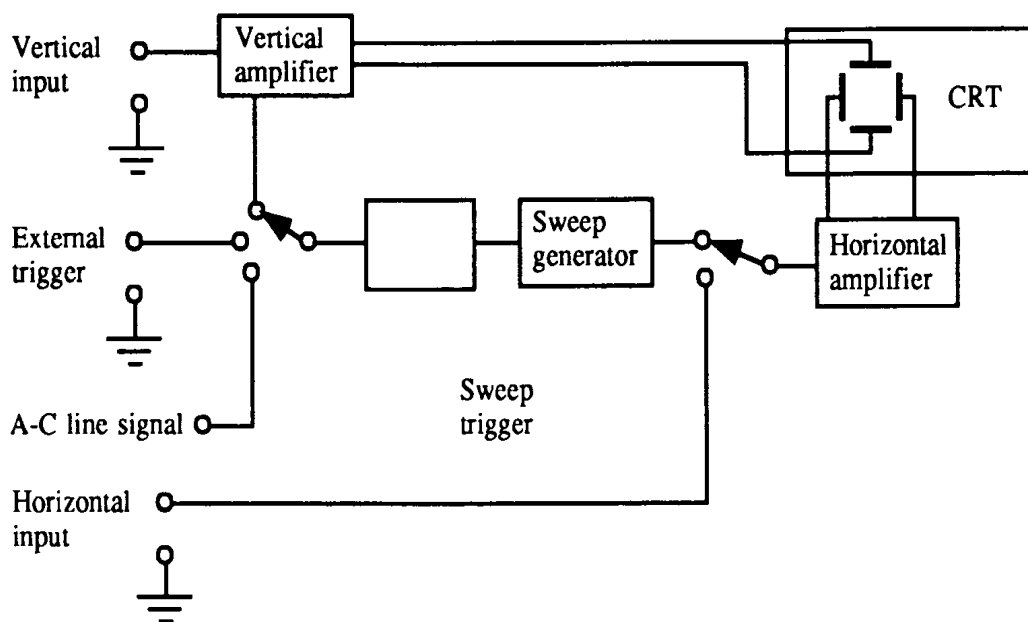


Figure 3. Block diagram of a typical oscilloscope.

### CRO Controls:

The controls available on most oscilloscopes provide a wide range of operating conditions and thus make the instrument especially versatile.

1. On-off switch.
2. INTENSITY. This is the intensity control connected to the grid G to control the beam intensity and hence the brightness of the screen spot.
3. AMPL/DIV. is a control of the Y (i.e. vertical) amplitude of the signal on the screen. (There is one of these for each channel).
4. AC/DC switch. This should be left in the DC position unless you cannot get a signal on-screen otherwise. (There is one of these for each channel).
5. ALT/CHOP/ADD switch. This is used to display both input channels separately or to combine them into one.
6. +/- Switch. This is used to invert the B channel on the display.
7. X POSITION: This is used to adjust the horizontal position of the signals on the screen.
8. LEVEL: This is used to determine the trigger level; i.e. the point of the waveform at which the ramp voltage will begin in time-base mode.
9. X5- Switch when pressed inward gives 5 times magnitude of signal.
10. Time/Div: This selector controls the frequency at which the beam sweeps horizontally across the screen in time-base mode, as well as whether the oscilloscope is in time-base mode or XY mode. This switch has the following positions:
11. (a) X VIA A In this position, an external signal connected to input A is used in place of the internally generated ramp. (This is also known as XY mode.)

(b) .5, 1, 2, 5, etc. Here the internally generated ramp voltage will repeat such that each large (cm) horizontal division corresponds to .5, 1, 2, 5, etc. ms. or  $\mu$ s depending on the multiplier and magnitude settings.

12. CH-I/CH-II, TRIG-I/ TRIG-II: When out, select and trigger CH-I and when pressed, select and trigger CH-II

### CATHODE-RAY TUBE:

Power ON/OFF: Push button switch for supplying power to instrument.

Focus: Focus the spot or trace on the screen. It control sharpness of trace.

Intensity: Regulates the brightness of the spot or trace.

### VERTICAL AMPLIFIER SECTION

Position: Controls vertical positioning of oscilloscope display.

Sensitivity: Selects the sensitivity of the vertical amplifier in calibrated steps.

Variable Sensitivity: Provides a continuous range of sensitivities between the calibrated steps. Normally the sensitivity is calibrated only when the variable knob is in the fully clockwise position.

AC-DC-GND: Selects desired coupling (ac or dc) for incoming signal applied to vertical amplifier, or grounds the amplifier input. Selecting dc couples the input directly to the amplifier; selecting ac send the signal through a capacitor before going to the amplifier thus blocking any constant component.

### HORIZONTAL-SWEEP SECTION

Sweep time/cm: Selects desired sweep rate from calibrated steps or admits external signal to horizontal amplifier.

Sweep time/cm Variable: Provides continuously variable sweep rates. Calibrated position is fully clockwise.

Position: Controls horizontal position of trace on screen.

Horizontal Variable: Controls the attenuation (reduction) of signal applied to horizontal amplifier through Ext. Horiz. Connector.

### TRIGGER

The trigger selects the timing of the beginning of the horizontal sweep.

**Slope:** Selects whether triggering occurs on an increasing (+) or decreasing (-) portion of trigger signal.

**Coupling:** Selects whether triggering occurs at a specific dc or ac level.

**Source:** Selects the source of the triggering signal.

**INT** - (internal) - from signal on vertical amplifier

**EXT** - (external) - from an external signal inserted at the EXT.TRIG. I/P

**LINE** - 60 cycle trigger

**Level:** Selects the voltage point on the triggering signal at which sweep is triggered. It also allows automatic (auto) triggering or allows sweep to run free (free run).

## 1. Voltage Measurement-

Voltage is shown on the **vertical y-axis** and the scale is determined by the Y AMPLIFIER (VOLTS/CM) control. Usually **peak-peak voltage** is measured because it can be read correctly even if the position of 0V is not known. The **amplitude** is half the peak-peak voltage.

If you wish to read the amplitude voltage directly you must check the position of 0V (normally halfway up the screen): move the AC/GND/DC switch to GND (0V) and use Y-SHIFT (up/down) to adjust the position of the trace if necessary, switch back to DC afterwards so you can see the signal again.

**Voltage = distance in cm × volts/cm**

*Example: peak-peak voltage = 4.2cm × 2V/cm = 8.4V*

*amplitude (peak voltage) = 1/2 × peak-peak voltage = 4.2V*

## 2. Time period/ Frequency Measurement-


Time is shown on the **horizontal x-axis** and the scale is determined by the TIMEBASE (TIME/CM) control. The **time period** (often just called **period**) is the time for one cycle of the signal. The **frequency** is the number of cycles per second, *frequency = 1/time period*

- Ensure that the variable time-base control is set to 1 or CAL (calibrated) before attempting to take a time reading.

**Time = distance in cm × time/cm**

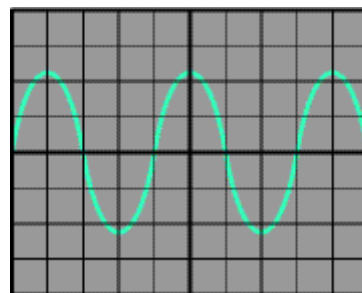*Example: time period = 4.0cm × 5ms/cm = 20ms*

*and frequency = 1/time period = 1/20ms = 50Hz*



Y AMPLIFIER: 2V/cm

TIMEBASE: 5ms/cm

**Example measurements:**

peak-peak voltage = 8.4V

amplitude voltage = 4.2V

time period = 20ms

frequency = 50Hz

**OBSERVATION TABLE:**

<i>S.No.</i>	<i>Input Frequency</i>	<i>Input Amplitude</i>	<i>Calculated Frequency</i>	<i>% error</i>

**RESULT** – Operating Principle and application of CRO have been studied.

## 2. FUNCTION GENERATOR

A **function generator** is a piece of electronic test equipment or software used to generate electrical waveforms. These waveforms can be either repetitive, or single-shot in which case some kind of triggering source is required (internal or external).

Another type of function generator is a sub-system that provides an output proportional to some mathematical function of its input; for example, the output may be proportional to the square root of the input.



Analog function generators usually generate a triangle waveform as the basis for all of its other outputs. The triangle is generated by repeatedly charging and discharging a capacitor from a constant current source. This produces a linearly ascending or descending voltage ramp. As the output voltage reaches upper and lower limits, the charging and discharging is reversed using a comparator, producing the linear triangle wave. By varying the current and the size of the capacitor, different frequencies may be obtained.

Most function generators also contain a non-linear diode shaping circuit that can convert the triangle wave into a reasonably accurate sine wave. It does so by rounding off the hard corners of the triangle wave in a process similar to clipping in audio systems.

A typical function generator can provide frequencies up to 20 MHz and uses a BNC connector, usually requiring a 50 or 75 ohm termination. Specialized RF generators are capable of gigahertz frequencies and typically use N-type output connectors.

Function generators, like most signal generators, may also contain an attenuator, various means of modulating the output waveform, and often the ability to automatically and repetitively "sweep" the frequency of the output waveform (by means of a voltage-controlled oscillator) between two operator-determined limits. This capability makes it very easy to evaluate the frequency response of a given electronic circuit.

### CONTROLS AND INDICATORS:

1. **POWER SWITCH**- Push the switch "ON" will light the LED to indicate power "ON".

- 2. FREQUENCY CONTROL KNOB** – Used to adjust the required frequency for selected range with the multiplication factor of 0.04 to 4.0.
- 3. SYNC OUTPUT** – The TTL level square signal Output synchronous with frequency of Main Output.
- 4. SWEEP OUTPUT**- Sweep signal is available regardless of position of SWEEP ON switch provided with Sweep Rate Knob.
- 5. MAIN OUTPUT** – Function Output signal provides normal mode or sweep mode output depending on mode selected. The maximum Output impedance is  $50\Omega$ .
- 6. AMPLITUDE KNOB**- The amplitude of signal can be adjusted from 0.1Vp-p to 20Vp-p at No Load. Pull the Knob to attenuate the signal 10 times.
- 7. DC OFFSET**- This Knob can apply a DC Offset to Main Signal. Turn the Knob clockwise for Positive Offset and anti-clockwise for Negative Offset.
- 8. SWEEP RATE** –This Knob is used to adjust the sweep rate from 5 seconds to 25 milliseconds. Also if this Knob is pulled, then Sweep mode operation will be ON.
- 9. SWEEP WIDTH** –This Knob is used to adjust the Sweep Width. When the knob is in “Push” condition, a Linear Sweep Output will be available and When Knob is in “Pull” condition, then LOG Sweep Output will be available.
- 10. FUNCTION SELECTOR SWITCH** – A rotary Switch for waveform selection.
- 11. FREQUENCY RANGE SELECTOR SWITCH** – A rotary Switch to select the range from 10Hz to 1MHz in 6 steps.
- 12. COUPLING SWITCH** – It is three way switch to select Internal / External High Frequency / External Low Frequency mode.
- 13. CMOS ADJUST KNOB** – For adjusting the CMOS level of SYNC Output while in CMOS mode. Pull the Knob for CMOS ON.
- 14. EXTERNAL INPUT BNC** – Connector for counting external signal frequency.
- 15. VCF INPUT BNC** – For connecting external DC or AC signal from 0 to 10V to achieve voltage controlled frequency output.

### FUNCTION GENERATOR OUTPUT:


1. Select the type of waveform required by rotary switch of FUNCTION.
2. Select the Range of frequency by rotary switch of RANGE.
3. Connect Main Output signal to Channel 1 of oscilloscope and Sync Output signal to Channel 2 of oscilloscope. Set the trigger source of oscilloscope at Channel 2.
4. Set the frequency of the signal by adjustment knob. The display shows the frequency reading of signal.
5. Adjust the amplitude of the signal Amplitude knob. Pull the knob if the signal is to be attenuated 10 times.
6. Set the DC Offset of signal by OFFSET knob to required level (-10V to +10V).
7. Check the impedance of the load before connecting (50W max.).

### PRECAUTIONS:

1. Before switching ON the device be familiar with its control knobs.
2. Operate control knobs smoothly.



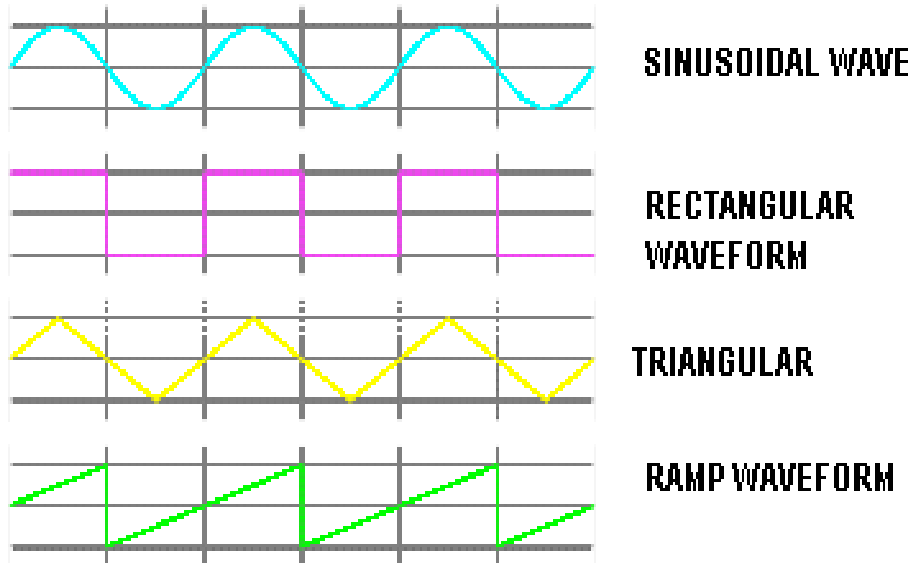3. Ensure position of calibrated/variable control knob at calibrated position.



**OUTPUT WAVEFORMS ON CRO**

## Multimeter

A **multimeter** or a **multitester**, also known as a **VOM** (Volt-Ohm meter), is an electronic measuring instrument that combines several measurement functions in one unit. A typical multimeter may include features such as the ability to measure voltage, current and resistance. Multimeters may use analog or digital circuits—**analog multimeters** (AMM) and **digital multimeters** (often abbreviated **DMM** or **DVOM**.) Analog instruments are usually based on a micro ammeter whose pointer moves over a scale calibrated for all the different measurements that can be made; digital instruments usually display digits, but may display a bar of a length proportional to the quantity being measured. A multimeter can be a hand-held device useful for basic fault finding and field service work or a bench instrument which can measure to a very high degree of accuracy. They can be used to troubleshoot electrical problems in a wide array of industrial and household devices such as electronic equipment, motor controls, domestic appliances, power supplies, and wiring systems.



### Power Supply

A **power supply** is a device that supplies electric power to one or more electric loads. The term is most commonly applied to devices that convert one form of electrical energy to another, though it may also refer to devices that convert another form of energy (mechanical, chemical, solar) to electrical energy. A regulated power supply is one that controls the output voltage or current to a specific value; the controlled value is held nearly constant despite variations in either load current or the voltage supplied by the power supply's energy source.

Every power supply must obtain the energy it supplies to its load, as well as any energy it consumes while performing that task, from an energy source

### Active Elements & Passive Elements


"The elements within a circuit will either control the flow of electric energy or respond to it. Those elements which control the flow of electric energy are known as active elements and those which dissipate or store the electric energy are passive elements."

"The three linear passive elements are the Resistor, the Capacitor and the Inductor. Examples of non-linear passive devices would be diodes, switches and spark gaps. Examples of active devices are Transistors, Triacs, Varistors, Vacuum Tubes, relays, solenoids and piezo electric devices."


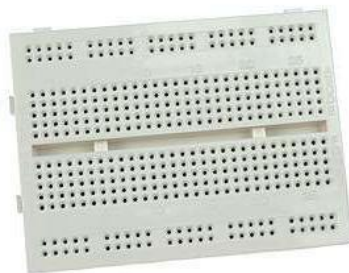
### Bread Board

A breadboard (protoboard) is a construction base for prototyping of electronics. The term is commonly used to refer to solderless breadboard (plugboard). Because the solderless breadboard does not require soldering, it is reusable. This makes it easy to use for creating temporary prototypes and experimenting with circuit design.



### RESULTS AND DISCUSSION:

Study of lab equipments- CRO, Multimeter, Function Generator, Power supply- Active, and Passive Components & Bread Board has been studied successfully.

### POST EXPERIMENT QUESTIONS:

1. What is the basic function of CRO and how it performs?
2. What is the basic function of Function Generator and how it performs?
3. What do you mean by active element and passive element ?
4. What is the purpose of the grid and X&Y-plates?
5. For a certain ac input signal, if the Volt/Div knob is set to a lower value, what effect does this have on the size of the signal on the screen?
6. What is the physical meaning of the root-mean-square value of an ac signal?

## ***EXPERIMENT NO.2***

**OBJECTIVE:** To study the PN junction diode characteristics under Forward & Reverse bias conditions.

### **APPARATUS & MATERIAL REQUIRED:**

S.No.	Component	Specifications	Quantity
1	R.P.S	0-30 V	1
2	Ammeter	0-100 $\mu$ A	1
3	Voltmeter	(0-1)V	1
4	Diode	IN4001	1
5	Resistor	1K $\Omega$	1
6	Wires		As Required

### **THEORY:**

A PN junction diode is a two terminal junction device. It conducts only in one direction (only on forward biasing).

#### **Forward bias:**

On forward biasing, initially no current flows due to barrier potential. As the applied potential exceeds the barrier potential the charge carriers gain sufficient energy to cross the potential barrier and hence enter the other region. The holes, which are majority carriers in the P-region, become minority carriers on entering the N-regions, and electrons, which are the majority carriers in the N-region, become minority carriers on entering the P-region. This injection of Minority carriers results in the current flow, opposite to the direction of electron movement.

#### **Reverse bias:**

On reverse biasing, the majority charge carriers are attracted towards the terminals due to the applied potential resulting in the widening of the depletion region. Since the charge carriers are pushed towards the terminals no current flows in the device due to majority charge carriers. There will be some current in the device due to the thermally generated minority carriers. The generation of such carriers is independent of the applied potential and hence the current is constant for all increasing reverse potential. This current is referred to as Reverse Saturation Current ( $I_0$ ) and it increases with temperature. When the applied reverse voltage is increased beyond the certain limit, it results in breakdown. During breakdown, the diode current increases tremendously.

### **PROCEDURE:**

**Forward bias:**


1. Connect the circuit as per the diagram.
2. Vary the applied voltage  $V$  in steps of  $0.1V$ .
3. Note down the corresponding Ammeter readings  $I_f$ .
4. Plot a graph between  $V_f$  &  $I_f$

**Reverse bias:**


1. Connect the circuit as per the diagram.
2. Vary the applied voltage  $V_r$  in steps of  $0.5V$ .
3. Note down the corresponding Ammeter readings  $I_r$ .
4. Plot a graph between  $V_r$  &  $I_r$

**CIRCUIT DIAGRAM:**


**FORWARD BIAS:**

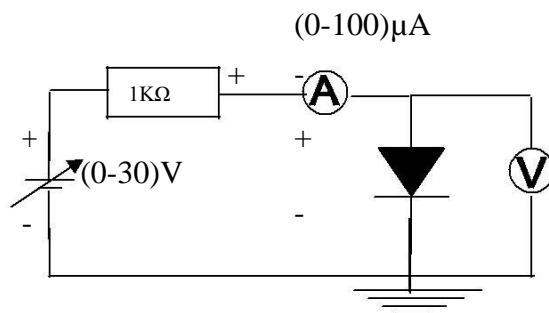

**REVERSE BIAS:**

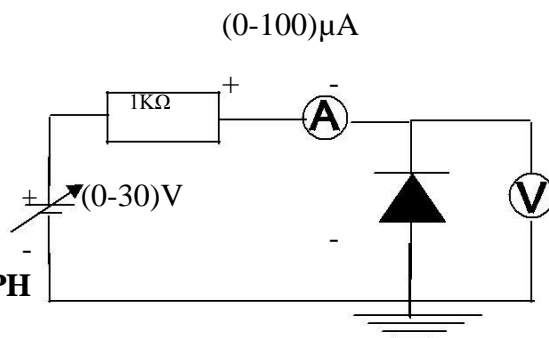

**MODEL GRAPH**

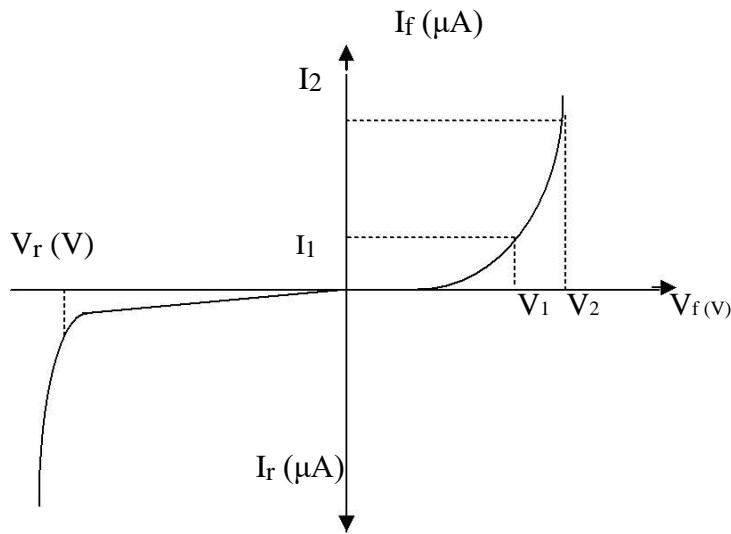

**Observation table:**

**Forward bias:**

S.No.	$V_f$	$I_f$

**reverse bias:**

S.No.	$V_r$	$I_r$

**RESULT:**

Forward and Reverse bias characteristics of the PN junction diode was Studied.

**PRECAUTIONS:**

- 1) Make the connections as per the circuit diagram carefully.
- 2) Observe the waveform carefully on the CRO.
- 3) The connections should be tight.

**POST- EXPERIMENT QUESTIONS:**

1. Name different types of diode capacitances.
2. Define peak inverse voltage.
3. What is the importance of barrier potential in diode?
4. Discuss the formation of depletion region.
5. Give the relationship between leakage current and temperature.

### **EXPERIMENT NO.3**


**OBJECTIVE:** To study the working of Half Wave and Full wave (Bridge Type) Rectifier.

**APPARATUS REQUIRED:** Cathode Ray Oscilloscope (CRO), Bread board, Transformer, diodes, resistors, connecting wires.

#### **THEORY:**


##### **Diode rectifier circuits**

The basic half-wave rectifier circuit is shown in Figure 1. The input signal  $V_{in}$  to the rectifier is assumed to be a purely AC signal with a time-average value of zero. Since current passes through an ideal diode only when the input signal is positive, the output signal  $V_{out}$  across the load resistor will be as shown below.

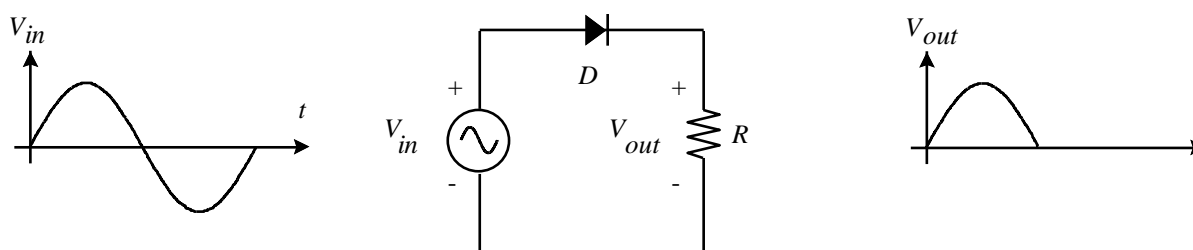

**Figure 1: Half-wave rectifier circuit and respective waveforms**


A half-wave rectifier can be connected to the transformer secondary as shown in Figure 2 to generate the typical half-wave output signal as discussed before. The half-wave rectifier circuit produces an output signal whose fundamental frequency is the same as the input AC signal.

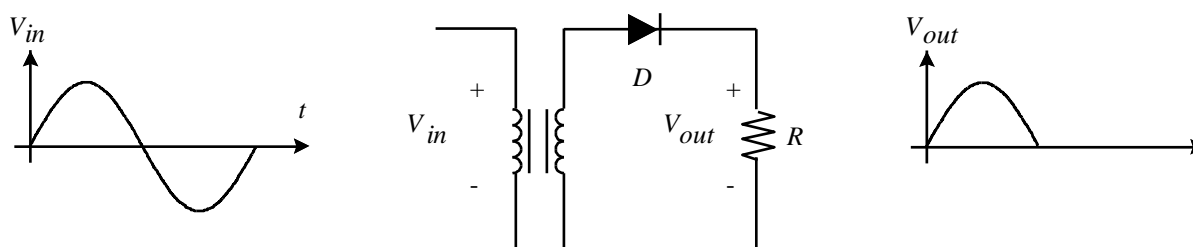

**Figure 2: Half-wave rectifier circuit using a transformer**

When input AC signal is applied across the bridge rectifier, during the positive half cycle diodes  $D_1$  and  $D_3$  are forward biased and allows electric current while the diodes  $D_2$  and  $D_4$  are reverse biased and blocks electric current. On the other hand, during the negative half cycle diodes  $D_2$  and  $D_4$  are forward biased and allows electric current while diodes  $D_1$  and  $D_3$  are reverse biased and blocks electric current.

During the positive half cycle, the terminal A becomes positive while the terminal B becomes negative. This causes the diodes  $D_1$  and  $D_3$  forward biased and at the same time, it causes the diodes  $D_2$  and  $D_4$  reverse biased.

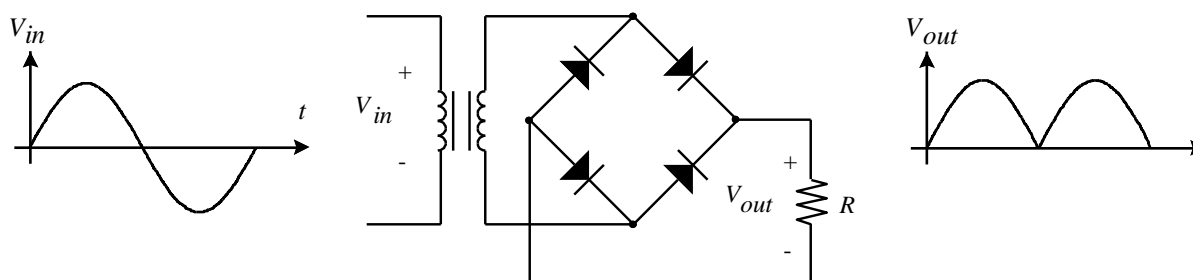

**Figure 3:**  
Full-wave  
rectifier  
using the  
bridge  
circuit

### PROCEDURE:

1. Connect the circuit as shown in the circuit diagram.
2. Connect the primary side of the transformer to AC mains and the secondary side to rectifier input.
3. Using a CRO, measure the maximum voltage  $V_m$  of the AC input voltage (at the anode) of the rectifier and AC voltage (at the cathode) at the output of the rectifier.
4. Using a DC voltmeter, measure the DC voltage at the load resistance.
5. Observe the Waveforms at the secondary windings of transformer and across load resistance for a load of  $1K\Omega$ .
6. Calculate the ripple factor ( $\gamma$ ), percentage of regulation and efficiency ( $\eta$ ) with the below given formulae.

### RESULT:

The application of diode as Rectifier circuits have been studied and input-output waveforms have been observed on the CRO.

### PRECAUTIONS:

1. Make the connections as per the circuit diagram carefully.
2. Observe the waveform carefully on the CRO.
3. The connections should be tight.

### POST EXPERIMENT QUESTIONS:

1. What is a Rectifier?
2. What is a Ripple Factor ( $\gamma$ ) and Efficiency ( $\eta$ )?
3. What is PIV and TUF?
4. What are the applications of rectifier?



## **EXPERIMENT NO.4**

**OBJECTIVE:** To study the application of diode as (i) Clipper circuit and (ii) Clamper Circuit.

### **APPARATUS & MATERIAL REQUIRED:**

S.No.	Component	Specifications	Quantity
1	CRO	25MHz	1
2	Function Generator	3MHz	1
3	Bread Board		1
4	DC Supply	0-5V	1
5	Diode	1N4007	1
6	Digital Multimeter		1
7	Resistors	4.7K $\Omega$ , 100K $\Omega$	Each 1
8	Capacitors	1 $\mu$ F,10V	1
9	Connecting wires & CRO Probes		As Required

### **THEORY:**

A clipper is a circuit with which the waveform is shaped by removing or clipping a portion of the applied input signal waveform without distorting the remaining part. Clippers fall into the general category of wave-shaping circuits. The function of a clipper is to limit the amplitude of a signal to some particular maximum positive or negative value. Clipper can remove signal voltages above or below a specified level.

**Clipper Circuits:** Clippers are networks which clip away part of the applied signal.

**Clippers are used to:**

- Create a specific type of signal.
- Limit the voltage that can be applied to a network.

**Clipper circuit consists of:**

- AC-source.
- Diode.
- DC-Source (to shift the operating point to the required value).

### **Clamper Circuits:**


Clamping circuits shifts or change a signal to different d.c. level. Clamping circuit introduces a d.c. level to an a.c signal. Clampers are networks that clamp the input signal to a different dc level, but the peak-to-peak swing of the applied signal will remain the same. Clamper circuit consists of clipper components plus capacitor.

### **CIRCUIT- DIAGRAMS:**

**Clipper Circuits:-**

This circuit limits an input voltage to certain minimum and maximum values. In the circuit in Figure-1, as long as  $V_i$  is less than  $V_{B1}$ , then the diode will be reverse biased (an open circuit). In this case, the output voltage will track the input voltage. If  $V_i$  exceeds  $V_{B1}$  then the diode turns on and then  $V_o$  will be  $V_{B1}$  thus


this circuit limits the output voltage to less than  $V_{B1}$ . By rearranging the components, variations on this circuit can be achieved.

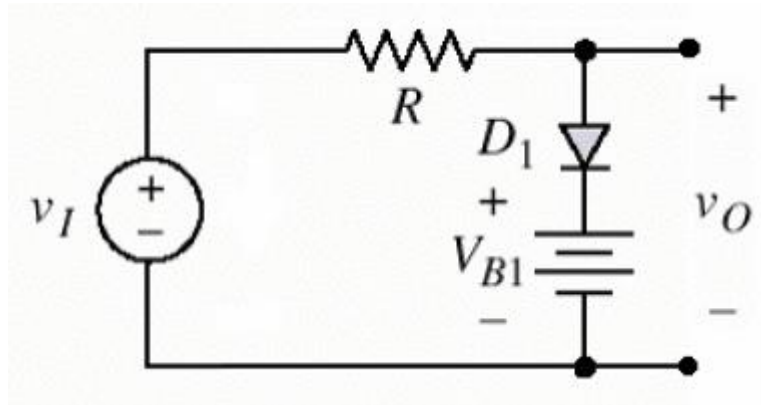

*Figure 1: Schematic of a clipper circuit.*
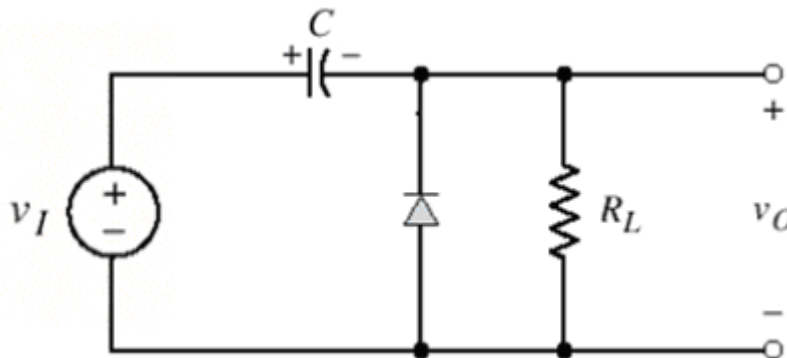
#### **Clamper Circuits:-**

This circuit works by allowing the capacitor to charge up and act like a battery. This is the voltage across the capacitor depends on the input waveform, the output maximum( or the minimum depending on the orientation of the diode) will be clamped to a fixed reference point .


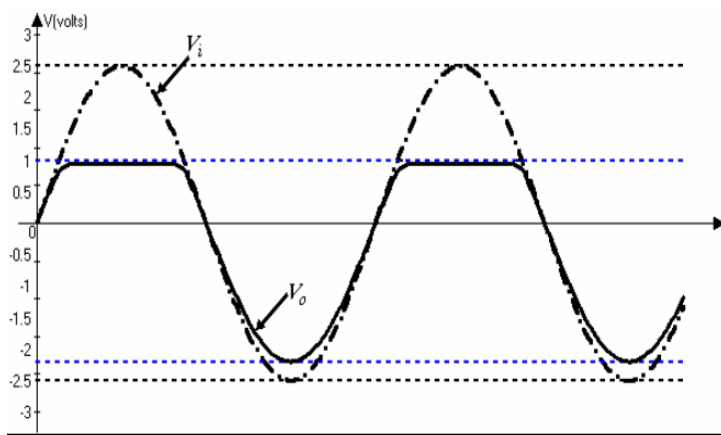


*Figure 2: Schematic of a clamper circuit.*

#### **PROCEDURE:**


#### **DIODE CLIPPER CIRCUITS:**

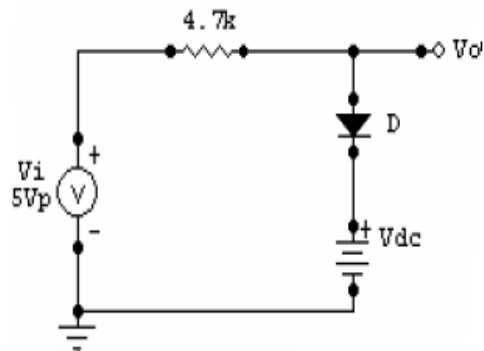1. Connect the circuit in Figure a. Use  $R = 100 \text{ K}\Omega$  and a 1N4007 diode. For the input signal  $v_I$ , use  $5V_{p-p}$ , 1KHz sine wave and use variable power supply to provide the battery voltage. Set  $V_B=1 \text{ V}$ . Measure and sketch the input and output waveforms.
2. Repeat the procedure for the remaining circuits. For Fig-d, set  $V_{B1}=0.5 \text{ V}$ ,  $V_{B2}=1 \text{ V}$ . Again verify Variable Supply Source output voltages using Voltmeter. Re-adjust if necessary. Observe the input and output waveforms on the CRO.



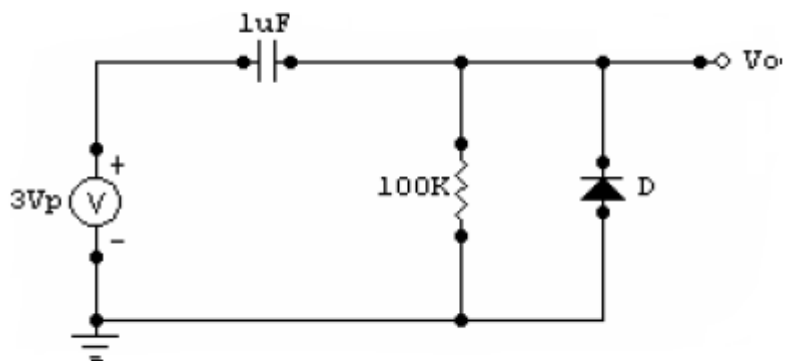
### DIODE CLAMPER CIRCUITS:

Connect the circuit as shown below in Fig.



The input and output waveforms are:

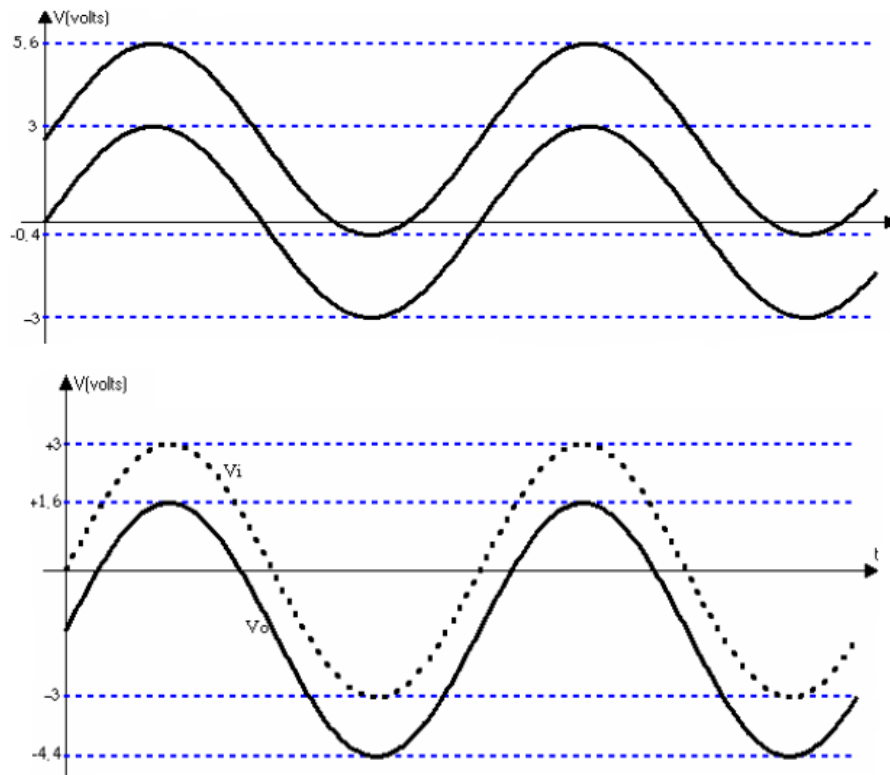

### RESULT:

The application of diode as Clipper and Clamper circuits have been studied and input-output waveforms have been observed on the CRO.

### PRECAUTIONS:

4. Make the connections as per the circuit diagram carefully.
5. Observe the waveform carefully on the CRO.
6. The connections should be tight.

### POST- EXPERIMENT QUESTIONS:

1. Name different types of clipper circuits.
2. What is the difference between series clipper and shunt clipper?
3. What are the types of clamper circuits?
4. Discuss the output waveforms from the clipper circuits. How do these waveforms differ from those expected if ideal diodes were used? Why?
5. What is the difference between clipping circuit and clamping circuit?


## **EXPERIMENT NO.5**

**OBJECTIVE:** To study the application of Zener diode as a voltage regulator.

### **APPARATUS & MATERIAL REQUIRED:**

S.No.	Component	Specifications	Quantity
1.	Zener diode	ZD-9V	01
2.	Bread board		01
3.	Variable DC supply	0-30V	01
4.	Multi-meter	200mV-1000V	01
5.	Resistors	1K $\Omega$ , 10K $\Omega$	Each 1
6.	Variable load (potentiometer)	10K $\Omega$	01

### **CIRCUIT DIAGRAM: -**

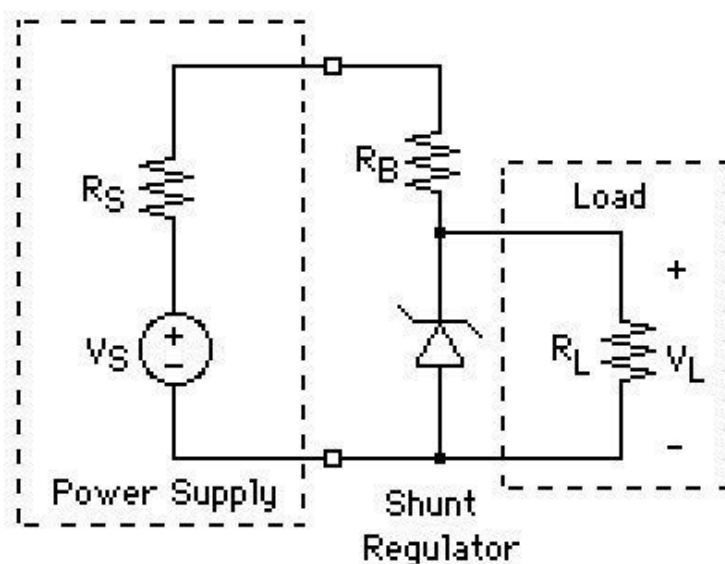

### **THEORY:**

#### **VOLTAGE REGULATION:-**

**Voltage Regulator:** A voltage regulator circuit is required to maintain a constant dc output voltage across the load terminals in spite of the variation:

- Variation in input mains voltage
- Change in the load current
- Change in the temperature

The voltage regulator circuit can be designed using Zener diode. For that purpose, Zener diode is operated always in reverse biased condition. Here, Zener is operated in break-down region and is used to regulate the voltage across a load when there are variations in the supply voltage or load current.

The figure shows the Zener voltage regulator, it consists of a current limiting resistor  $R_s$  connected in series with the input voltage  $V_s$  and Zener diode is connected in parallel with the load  $R_L$  in reverse biased condition. The output voltage is always selected with a breakdown voltage  $V_Z$  of the diode.

The input source current,  $I_s = I_z + I_L$ ..... (1)

The drop across the series resistance,  $R_s = V_{in} - V_z$  ..... (2)

And current flowing through it,  $I_s = (V_{in} - V_z) / R_s$  ..... (3)

From equation (1) and (2), we get,  $(V_{in} - V_z) / R_s = I_z + I_L$  ..... (4)

**Regulation with a varying input voltage (line regulation):** It is defined as the change in regulated voltage with respect to variation in line voltage. It is denoted by 'LR'.

In this, input voltage varies but load resistance remains constant hence, the load current remains constant. As the input voltage increases, from equation (3)  $I_s$  also varies accordingly. Therefore, Zener current  $I_z$  will increase. The extra voltage is dropped across the  $R_s$ . Since, increased  $I_z$  will still have a constant  $V_z$  and  $V_z$  is equal to  $V_{out}$ . The output voltage will remain constant. If there is decrease in  $V_{in}$ ,  $I_z$  decreases as load current remains constant and voltage drop across  $R_s$  is reduced. But even though  $I_z$  may change,  $V_z$  remains constant hence, output voltage remains constant.

## PROCEDURE:

- Connect the circuit as per the figure.
- Disconnect load and take reading of voltage at no load.
- Now connect load and vary the input voltage and take reading of the  $V_{out} = V_z$  i.e. voltage across load. Also measure the current.
- Calculate voltage regulation from the observation table. Now apply constant output voltage at input terminal and vary the load, measure the voltage across load.

$$\% \text{ Regulation} = \frac{V_{\text{no-load}} - V_{\text{full-load}}}{V_{\text{full-load}}}$$

## OBSERVATION TABLE:

- Fix the load at 10 K $\Omega$

S.No	$V_{in}$ (input voltage)	$R_L$	$V_{out} = V_z$

- Fix the input at  $V_z$

Sr. No.	$V_{in}$ (input voltage)	$R_L$	$V_{out} = V_z$

## RESULT:

The regulation of zener diode as a voltage regulator under the load of 10 K $\Omega$  is equal to.....

### **PRECAUTIONS:**

1. Check the circuit connection before giving supply.
2. Do not retain more reverse voltage for longer time.

### **POST EXPERIMENT QUESTIONS:-**

1. Define the phenomenon of 'Zener breakdown'.
2. Why Zener is suitable for voltage regulation?
3. What is voltage regulator? What is the need of it?
4. What is need of voltage regulation?
5. What are zener and avalanche break down?
6. What is effect of temperature on zener and avalanche break down?

### **EXPERIMENT NO.6**

**OBJECTIVE:** To study the input and output characteristics of a bipolar junction transistor in Common Emitter configuration

**APPARATUS & MATERIAL REQUIRED:**

S. No	Apparatus	Type	Range	Quantity
01	Transistor	BC147		1
02	Resistance		1k ohm, 10% tolerance, 1/2 watt rating	2
03	Regulated power supply		(0 – 30V), 2A Rating	2
04	Ammeter	MC	(1-30)mA, (0-500) $\mu$ A	1
05	Voltmeter	MC	(0 – 1)V, (0 – 30)V	1
06	Bread board and connecting wires			

**Theory:**

Bipolar junction transistor (BJT) is a 3 terminal (emitter, base, collector) semiconductor device. There are two types of transistors namely NPN and PNP. It consists of two P-N junctions namely emitter junction and collector junction.


In Common Emitter configuration the input is applied between base and emitter and the output is taken from collector and emitter. Here emitter is common to both input and output and hence the name common emitter configuration. Input characteristics are obtained between the input current and input voltage taking output voltage as parameter. It is plotted between  $V_{BE}$  and  $I_B$  at constant  $V_{CE}$

in CE configuration.


Output characteristics are obtained between the output voltage and output current taking input current as parameter. It is plotted between  $V_{CE}$  and  $I_C$  at constant  $I_B$  in CE configuration.

**Pin Assignment:**



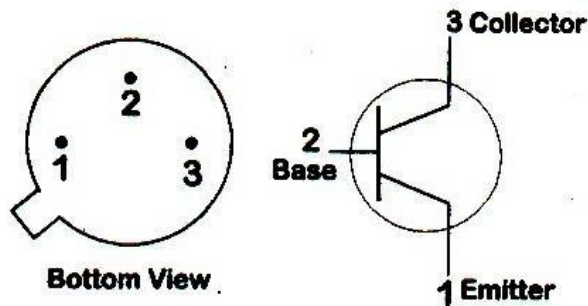

### Circuit Diagram:

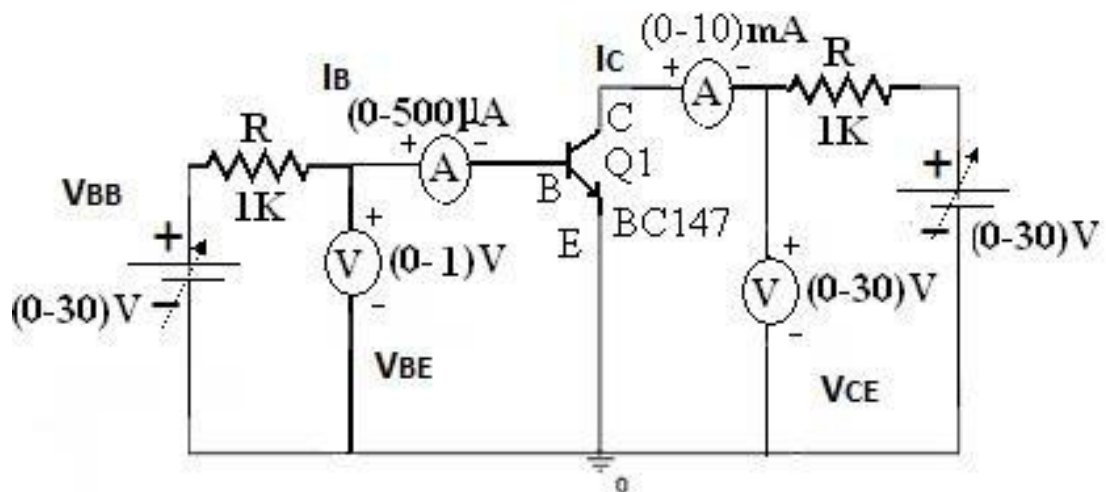

### PROCEDURE:

#### Input Characteristics

1. Connect the transistor in CE configuration as per circuit diagram
2. Keep output voltage  $V_{CE} = 0V$  by varying  $V_{CC}$ .
3. Varying  $V_{BB}$  gradually, note down both base current  $I_B$  and base - emitter voltage ( $V_{BE}$ ).
4. Repeat above procedure (step 3) for various values of  $V_{CE}$

#### Output Characteristics

1. Make the connections as per circuit diagram.
2. By varying  $V_{BB}$  keep the base current  $I_B = 20\mu A$ .

3. Varying  $V_{CC}$  gradually, note down the readings of collector-current ( $I_C$ ) and collector- emitter voltage ( $V_{CE}$ ).
4. Repeat above procedure (step 3) for different values of  $I_E$

### OBSERVATION TABLE:

#### Input Characteristics:

$V_{CE} = 0V$		$V_{CE} = 4V$	
$V_{BE}$ (volts)	$I_B$ (mA)	$V_{BE}$ (volts)	$I_B$ (mA)



### **Result:**

Thus the input and output characteristics of BJT in CE configuration was verified and the graph was plotted.

### **PRECAUTIONS:**

1. The readings should be taken properly.
2. The connections should be proper.

### **Post Experiment Questions**

1. Why is base width small?
2. Why is Silicon transistor more commonly used compared to Germanium transistor?
3. What is base width modulation?
4. The junction capacitance across collector to base junction is much lower than that across base to emitter junction. Why?
5. What is the difference between diffusion capacitance and transition capacitance?
6. What is the voltage across the collector to emitter terminal when the transistor is in (i) saturation (ii) cut-off (iii) active region?

## **EXPERIMENT NO.7**

**OBJECTIVE:** To study V-I characteristics of JFET

### **APPARATUS & MATERIAL REQUIRED:**

S.No.	Component	Specification	Quantity
1.	Bread board		01
2.	Dual Power supply	0-30V	02
3.	Multi-meter	200mV-1000V	01
4.	FET	BFW-10	01
5.	Connecting Wires		As Required

### **CIRCUIT DIAGRAM:**


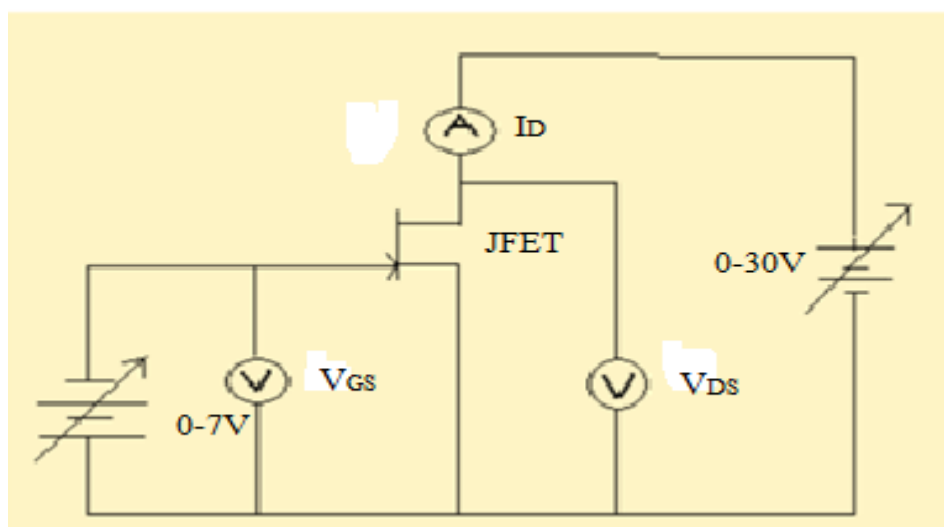


Fig 1: Circuit diagram of JFET
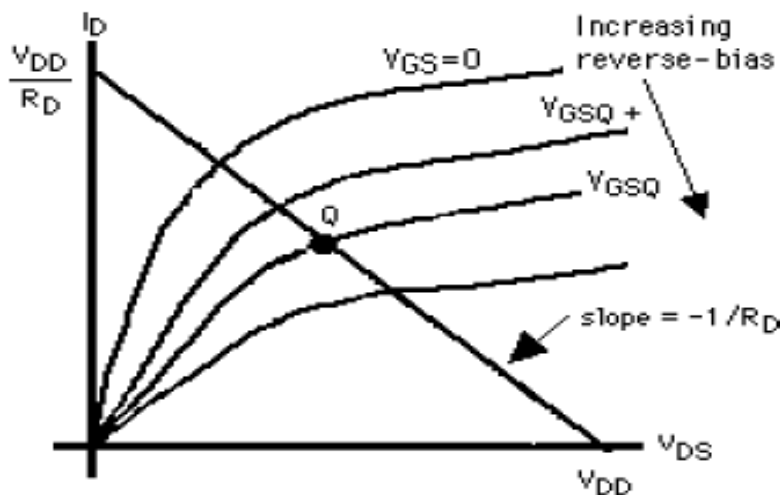
### **THEORY:**

A field-effect transistor is a unipolar, three terminal device. Its function depends only upon one type of carrier. Unlike BJT, a FET has high input impedance. This is a great advantage over BJT in switching operations. A FET can be either a JFET or MOSFET. Again a JFET can either have N-channel or P-channel. An N-channel JFET has an N –type semiconductor bar, two ends of which make the drain and source terminals. On the two sides of bar, PN junctions are made. These P regions make gates. Usually these two gates are connected

together form a single gate. The gate is given a negative bias with respect to the source. The drain is given a positive potential with respect to the source. In case of P-channel JFET, the terminals of all the batteries are reversed.



### OPERATION OF FET:

When the drain is positive and gate is negative, then P-N junction toward drain side is reverse biased. Therefore, depletion region will be more extended on this side than towards source side. When depletion region increases, drain current  $I_D$  increases. Such a value of gate voltage which makes  $I_D = 0$  is called pinch-off voltage. At this stage, depletion regions touch each other and block the channel.

### PROCEDURE:

1. Make the circuit connection as shown in the diagram.
2. Fix the voltage  $V_{GS}$  at some value: say 0V. Increase the drain voltage  $V_{DS}$  slowly in steps. Note drain current  $I_D$  for each step. Now change  $V_{GS}$  to another value and repeat the above. This way takes readings for 3 to 4 gate voltage values.
3. Plot the drain characteristics (graph between  $I_D$  and  $V_{DS}$  for fixed values of  $V_{GS}$ )
4. Calculate the FET parameters, as defined above from the characteristic curve.

## OBSERVATIONS:

Observation table for output Characteristics of FET

Sr. No.	$V_{gs} = 0\text{ V}$		$V_{gs} = \_\_\text{ V}$		$V_{gs} = \_\_\text{ V}$	
	$V_{DS}$ in V	$I_D$ in amp	$V_{DS}$	$I_D$	$V_{DS}$	$I_D$
1.						
2.						
3.						
4.						
5.						
6.						
7.						
8.						
9.						
10.						
11.						
12.						

## RESULTS

The drain characteristics of the FET are plotted on the graph.

## PRECAUTIONS:

1. The readings should be taken properly.
2. The connections should be proper.

## POST EXPERIMENT QUESTIONS:

1. Why FET is called as a unipolar device?
2. Justify: JFET is a voltage controlled device.
3. What is meant by “pinch-off” in JFET?
4. Why FET is advantageous than bipolar transistor?
5. Why wedge shaped depletion region is formed in FET under reverse bias gate condition?
6. Discuss the output and transconductance characteristics of JFET.
7. What are the applications of JFET?

## ***EXPERIMENT NO.8***

**OBJECTIVE:** To study V-I characteristics of MOSFET

### **APPARATUS & MATERIAL REQUIRED:**

S.No.	Component	Specification	Quantity
1.	Bread board		01
2.	Dual Power supply	0-30V	02
3.	Multi-meter	200Mv-1000V	01
4.	MOSFET	2N 7000	01
5.	Connecting Wires		As Required

### **THEORY:**

The Metal Oxide Semiconductor Field Effect Transistor (**MOSFET**) is a device used to amplify or switch electronic signals. It is a unipolar, unidirectional, voltage controlled device.

Operation:

Case 1: Gate is kept open.

The negative voltage applied to source terminal will make Pn+ junction forward bias. The positive voltage applied to drain terminal will make Pn+ junction reverse bias. Therefore there will not be any drain current.

Case 2: Positive potential is applied to gate

Here the gate terminal will act as positive plate of capacitor and P-substrate acts as another plate of capacitor.

When gate is kept at +ve potential, automatically the other plate induces negative charges this forms a channel (path) for electrons to move from drain terminal to source terminal.

Thus the application of gate source voltage controls the flow of drain current.

### **CIRCUIT DIAGRAM:**




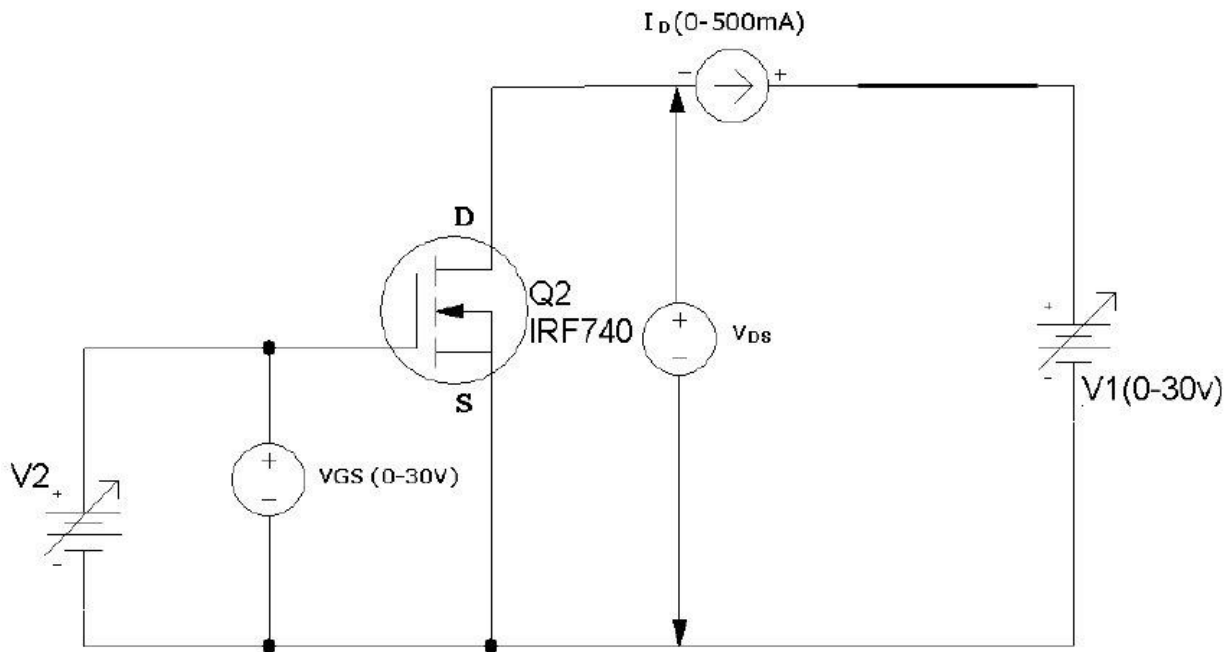


Fig 1: Circuit diagram of MOSFET

### Ideal Graphs:-

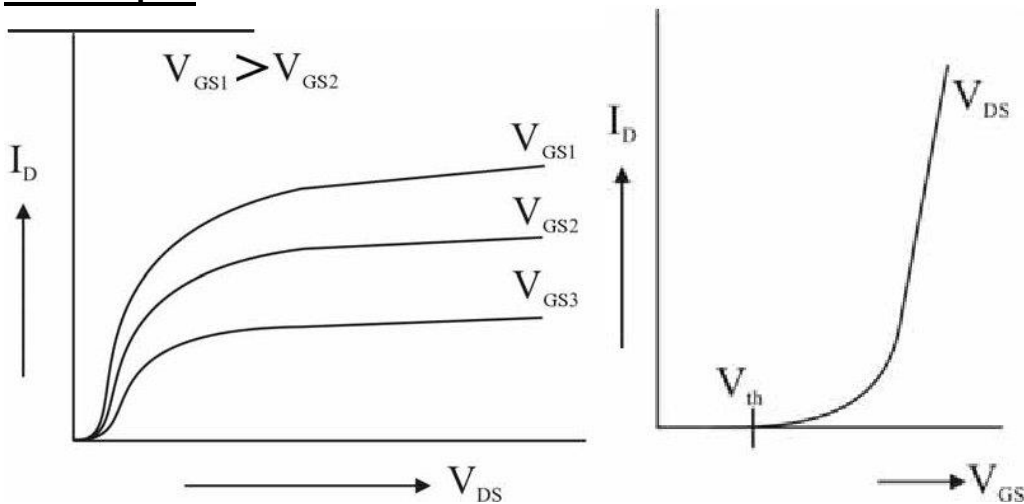

### **PROCEDURE:**

#### **Drain Characteristics:-**

1. Connections are made as shown in the circuit diagram.
2. Adjust the value of  $V_{GS}$  slightly more than threshold voltage  $V_{th}$
3. By varying  $V_1$ , note down  $I_D$  &  $V_{DS}$  and are tabulated in the tabular column
4. Repeat the experiment for different values of  $V_{GS}$  and note down  $I_D$  v/s  $V_{DS}$
5. Draw the graph of  $I_D$  v/s  $V_{DS}$  for different values of  $V_{GS}$ .

## Transconductance Characteristics:-

1. Connections are made as shown in the circuit diagram.
2. Initially keep  $V_1$  and  $V_2$  zero.
3. Set  $V_{DS} = \text{say } 0.6 \text{ V}$
4. Slowly vary  $V_2$  ( $V_{GE}$ ) with a step of 0.5 volts, note down corresponding  $I_D$  and  $V_{DS}$  readings for every 0.5v and are tabulated in the tabular column.
5. Repeat the experiment for different values of  $V_{DS}$  & draw the graph of  $I_D$  v/s  $V_{GS}$ .
6. Plot the graph of  $V_{GS}$  v/s  $I_D$

## Table:-

$V_{GS}(V)=$	
$V_{DS}(V)$	$I_D(mA)$

$V_{GS}(V)=$	
$V_{DS}(V)$	$I_D(mA)$

## RESULTS:

The drain characteristics of the FET are plotted on the graph.

## PRECAUTIONS:

1. Ensure connections as per the circuit diagram
2. Ensure polarity connection of power supply before switching ON power supply.

## POST EXPERIMENT QUESTIONS:

1. Why MOSFET is advantageous than JFET?
2. What is the need for High Impedance in MOSFET?
3. Discuss different types of MOSFET. What are the main difference between them?
4. State advantages, disadvantages and applications of MOSFET.
5. What are the similarities and differences between FET and MOSFET?
6. In MOSFET devices the N-channel type is better the P-channel type. How?
7. Interpret transfer characteristics from the given drain characteristics for MOSFET.

### ***EXPERIMENT NO.9***

**OBJECTIVE:** To verify characteristics of op-Amp and realization of Op-Amp as adder & subtractor

#### **APPARATUS & MATERIAL REQUIRED:**


S.No.	Component	Specifications	Quantity
1.	IC 741		01
2.	Resistors	1 K $\Omega$ , 100 $\Omega$ , 10K $\Omega$	05
3.	DC supply	0-30V	01
4.	Fixed dc supply	12V	01
5.	Multimeter	200mV-1000V	01
6.	CRO	25MHz	01
7.	Function generator	3MHz	01
8.	Breadboard		01
9.	Connecting wires	-	As required

#### **THEORY:**

Operational Amplifier (Op-Amp) is a differential amplifier and can perform mathematical operations such as addition, subtraction, etc. This is an integrated circuit (IC). In this experiment, we will be familiar with the 741 Op-Amp and study its applications as comparator, integrator and adder.
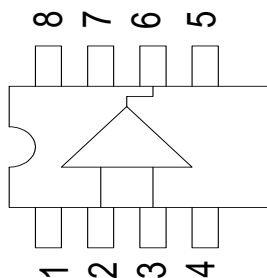
#### **THE 741 Op-Amp**


The block diagram of the 741 Op-Amp is shown in Fig. It has 8 pins (legs). To identify the pins of the 741 Op-Amp in the laboratory, place the Op-Amp on the bread-board in such a way that the **notch** is in your left side. Then the pin number should be identified as shown in following fig.



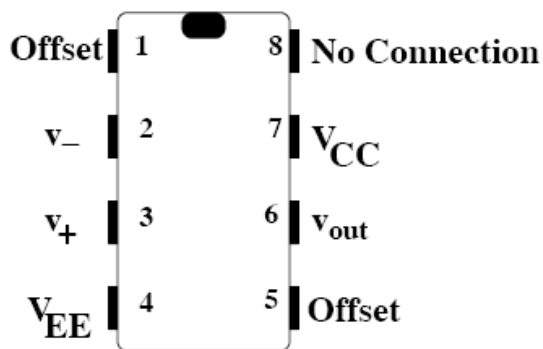**Pin diagram of the 741 Op-Amp**

The names of different pins are as follows

- 1 → offset null (usually not used)
- 2 → inverting input terminal
- 3 → non-inverting input terminal
- 4 → negative DC power supply (usually 5-15V negative)
- 5 → offset null (usually not used)
- 6 → output terminal
- 7 → positive DC power supply (usually 5-15V positive)
- 8 → not connected (NC)



## 1. Adder

### CIRCUIT DIAGRAM:

**Adder (Summing Amplifier):** Op-amp may be used to perform summing operation of several input signals in inverting inverting and non-inverting mode. The input signals to be summed up are given to inverting terminal or non-inverting terminal through the input resistance to perform inverting and non-inverting summing operations respectively. If the input to the inverting amplifier is increased, the resulting circuit is known as adder. Output is a linear summation of number of input signals. Each input signal produces a component of the output signal that is completely independent of the other input signal. When there are two inputs i.e.  $V_o = -(V_1 + V_2)$  This is the inverted algebraic sum of all the inputs. If we connect the inputs to non inverting terminal then the adder is non inverting adder.

**Subtractor:** The basic difference amplifier can be used as a subtractor. The signals to be subtracted are connected to opposite polarity inputs i.e. in inverting or non-inverting terminals of the op-amp. A circuit that finds the difference between two signals is called a subtractor.

### CIRCUIT DIAGRAM:

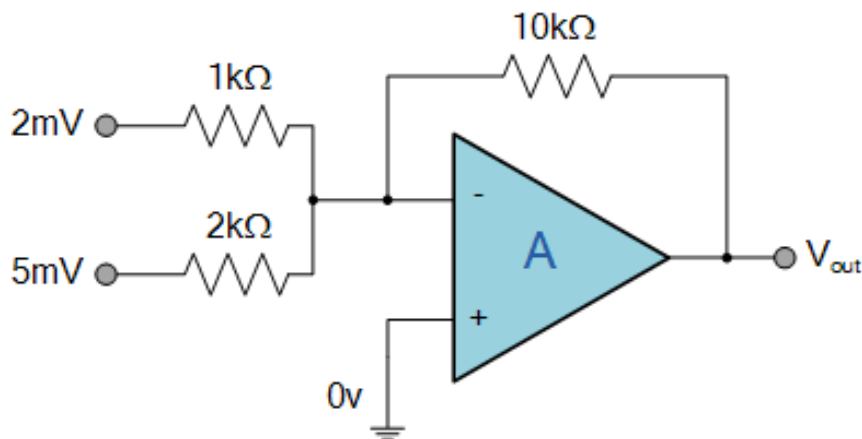


Fig.: Adder

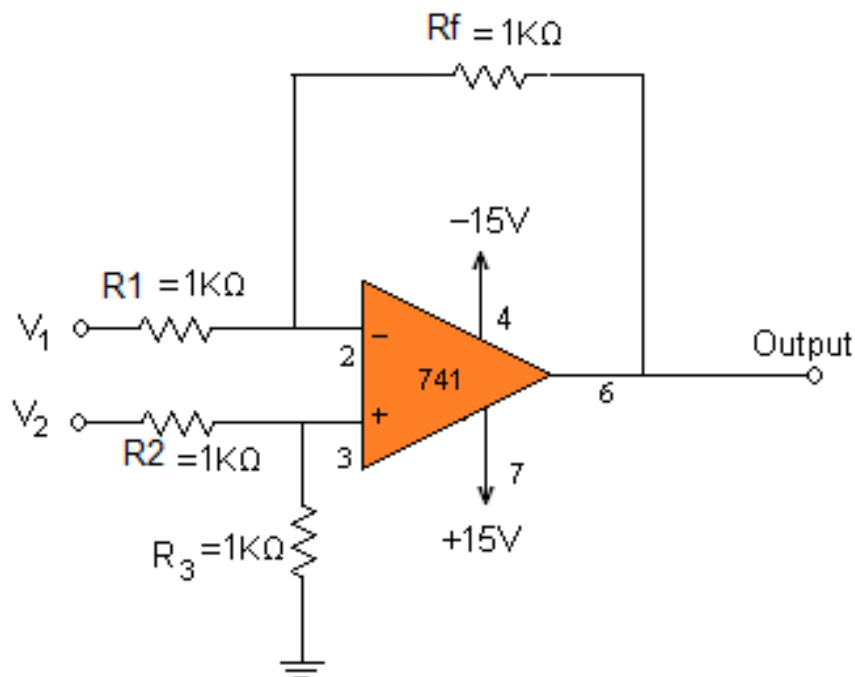


Fig.:Subtractor

**PROCEDURE:**

1. Connect the circuit according to the diagram and switch on the power supply.
2. Supply the input signal to the input terminal of the op amp circuit.
3. Observe the output waveform on the CRO.

**OBSERVATION TABLE:**

S.No	Amplitude of One I/P signal	Amplitude of another I/P signal	Amplitude of O/P signal

**RESULT:** Adder and subtractor of Op-Amp is verified.

**PRECAUTIONS:**

1. IC pin should be connected carefully.

2. Connections should be proper.
3. Common terminal of  $\pm 12\text{V}$  fixed DC supply should be used as ground.

### POST EXP. QUESTIONS:

- 1) What is an operational amplifier?
- 2) What are the four basic building blocks of an op-amp?
- 3) What is meant by input & output offset voltage of an op-amp?
- 4) Define the term: open loop and close loop gain.
- 5) What are the characteristics of ideal OP-AMP.
- 6) Define: CMRR, Slew-Rate and differential amplifier?
- 7) Draw the voltage transfer curve of an op-amp?

## **EXPERIMENT NO.10**


**OBJECT:** Verification and interpretation of truth tables for AND, OR, NOT, NAND, NOR, Exclusive OR (EX-OR), Exclusive NOR (EX-NOR) Gates.

**APPARATUS:** Bread board, logic gates ICs, wires.

**THEORY:** Logic gates are electronic circuits which perform logical functions on one or more inputs to produce one output. There are seven logic gates. When all the input combinations of a logic gate are written in a series and their corresponding outputs written along them, then this input/ output combination is called **Truth Table**. Various gates and their working is explained here.

### **AND Gate**

AND gate produces an output as 1, when all its inputs are 1; otherwise the output is 0. This gate can have minimum 2 inputs but output is always one. Its output is 0 when any input is 0.

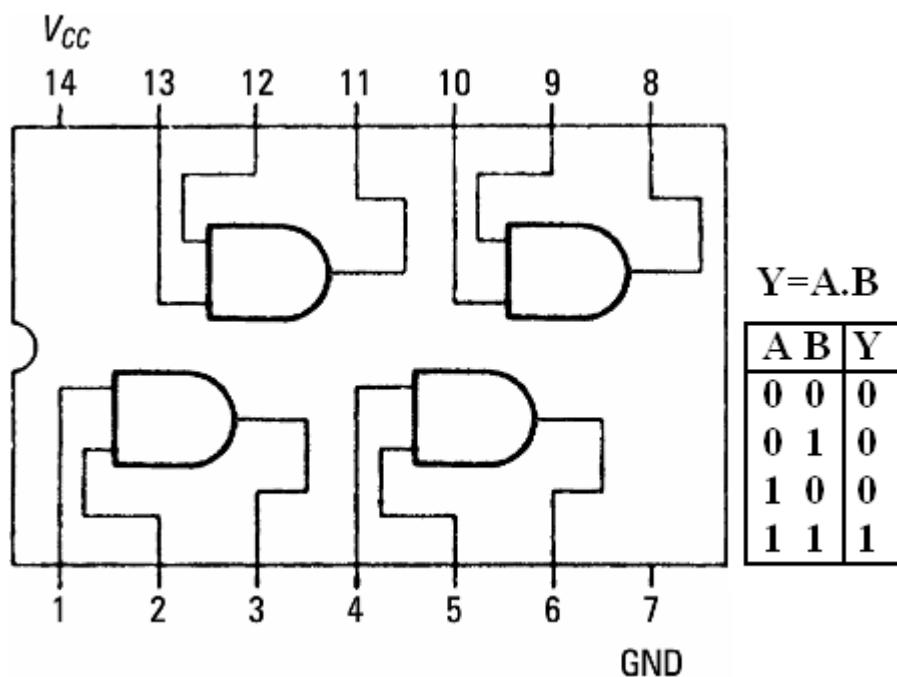


**IC 7408**

### **OR Gate**

OR gate produces an output as 1, when any or all its inputs are 1; otherwise the output is 0. This gate can have minimum 2 inputs but output is always one. Its output is 0 when all input are 0.




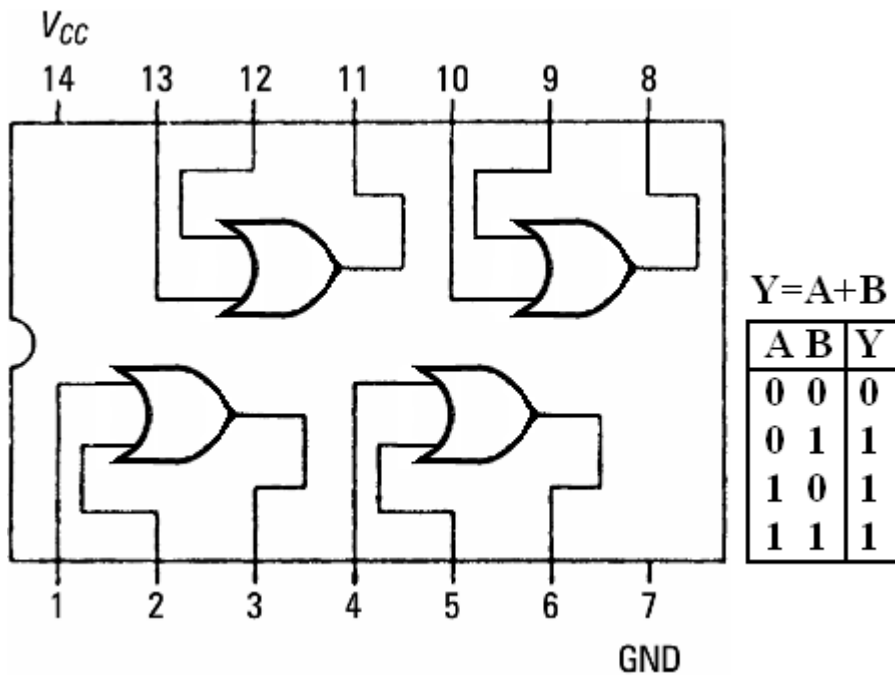

IC 7432

### NOT Gate


NOT gate produces the complement of its input. This gate is also called an INVERTER. It always has one input and one output. Its output is 0 when input is 1 and output is 1 when input is 0.

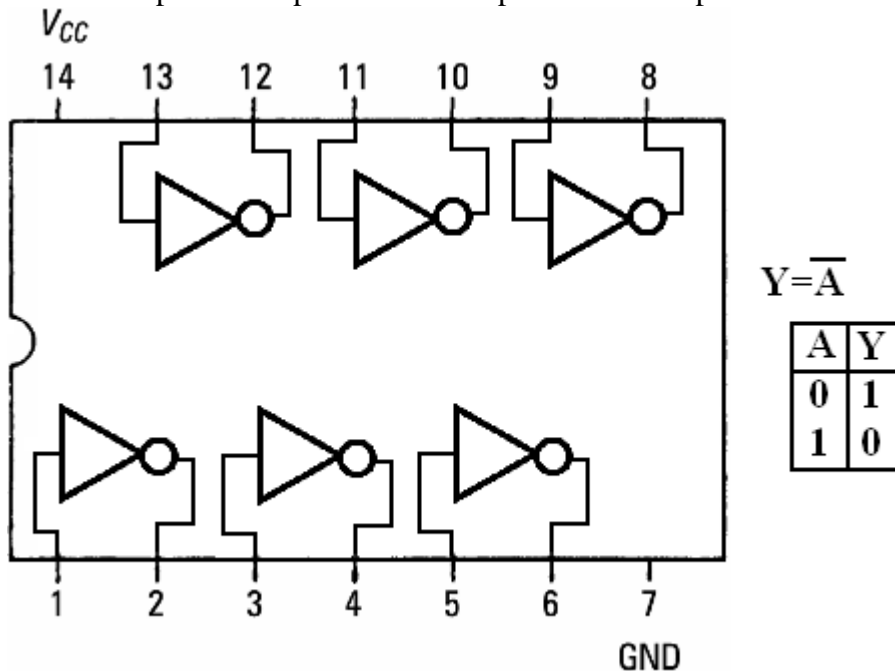

IC 7404

## NAND Gate


NAND gate is actually a series of AND gate with NOT gate. If we connect the output of an AND gate to the input of a NOT gate, this combination will work as NOT-AND or NAND gate. Its output is 1 when any or all inputs are 0, otherwise output is 1.

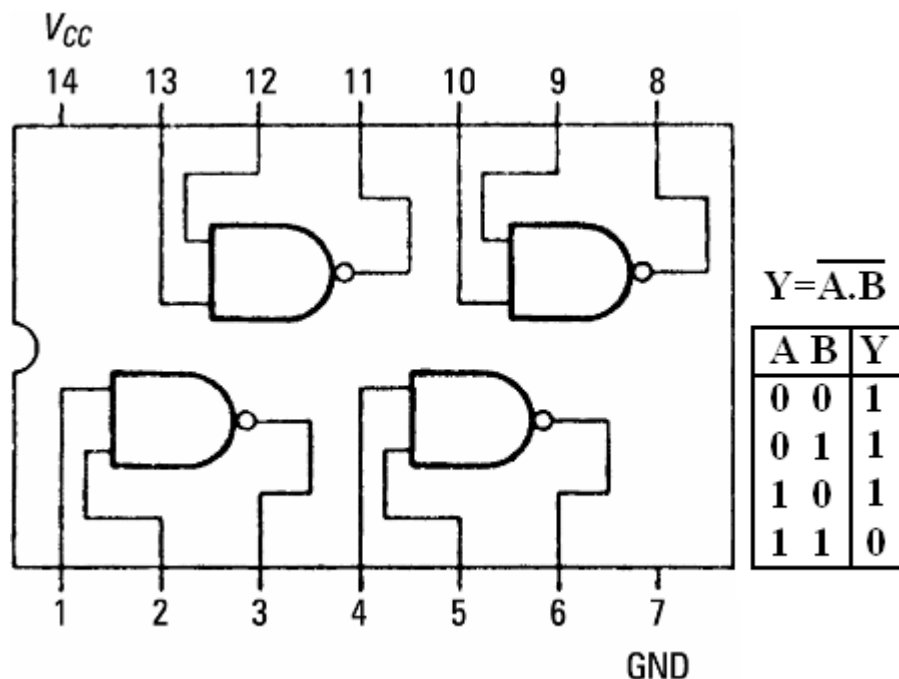

**IC 7400**

## NOR Gate

NOR gate is actually a series of OR gate with NOT gate. If we connect the output of an OR gate to the input of a NOT gate, this combination will work as NOT-OR or NOR gate. Its output is 0 when any or all inputs are 1, otherwise output is 1.

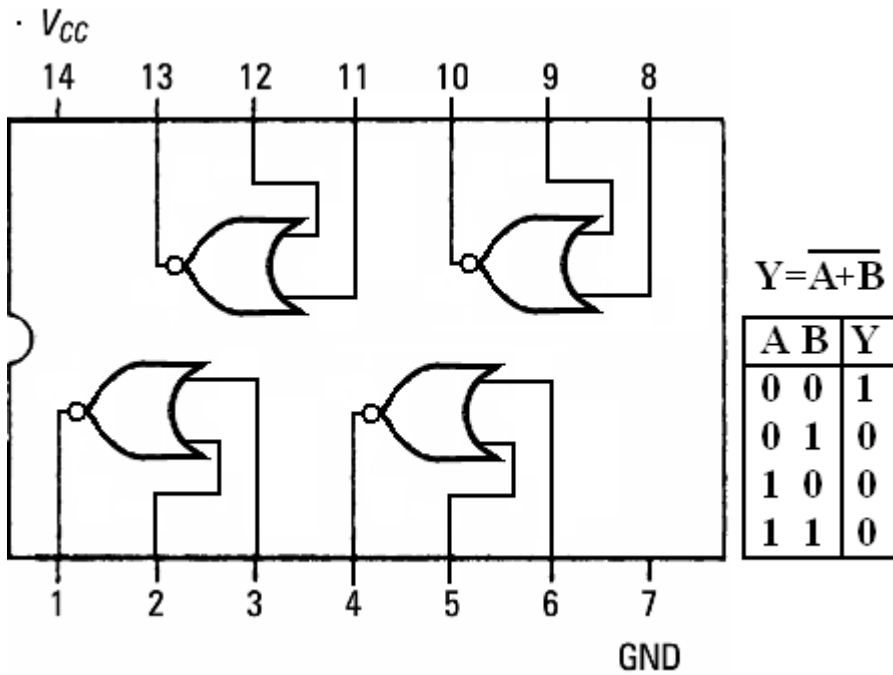

**IC 7402**

**Procedure:**

1. Make the connection on bread board according to the connection of IC..
2. Connect the inputs of any one logic gate to the logic sources and its output to the logic indicator.
3. Apply various input combinations and observe output for each one.
4. Verify the truth table for each input/ output combination.
5. Repeat the process for all other logic gates.
6. Switch off the ac power supply.

**Result:** Truth table of all gates are verified.

**PRECAUTIONS:**

1. IC pin should be connected carefully.
2. Connections should be proper.
3. Negative terminal of 5V fixed DC supply should be used as ground.

**POST EXP. QUESTIONS:**

1. What do you mean by logic gates?
2. What is universal gate and why named so?
3. Explain hybrid gates.
4. Implement XOR and XNOR gate with the help of NAND only and NOR only.

## LIST OF EQUIPMENTS

S.No.	Name of Equipment	Make	Qty. (No.)	Date of Purchase	Bill No.	Equipment Cost ( ₹ )
1	CRO Demonstrator (ScienTech,ST2001E,Sr. No. 0300333)	Scien Tech	1	3/8/2000	866	25000
2	CRO (ScienTech,ST 201,Sr. No.07008145,8253) Dual Trace 20 MHz	Scien Tech	2	3/8/2000	866	35680
3	CRO (ScienTech, ST 201,Sr. No. 100111368, 100111365 ) Dual Trace 20 MHz	Scien Tech	2	1/11/2001	1372	34220
4	CRO (Scien Tech, ST251,Sr.No. 0503439,0503441,45,0603456) 4 Trace 25 MHz	Scien Tech	4	23/7/2003	SE/IN/03-04/117	67680
5	CRO (Scien Tech, ST251,Sr.No. 8041344,09041376) 4 Trace 25 MHz	Scien Tech	2	29/9/2004	SE/IN/03-04/227	33088
6	CADDO 803 30 MHz Two Channel 4 Trace Microcontroller Oscilloscope with LCD Display (10082860,866)	Scien Tech	2	4/11/2008	RI/IN/08-09/162	34126
7	Function Generator (ScienTech, SM 5071, Sr.No.02090132,) 3MHz	Scien Tech	1	12/10/2002	1605	9100
8	Function Generator (Scientific, HM 5030-4 Sr.No.992231,992238)	Scien tific	2	5/10/1999	164/90	13950
9	Function Generator (Scientific, HM 5060 Sr.No.0700319,0700320)	Scien tific	2	3/8/2000	866	14950
10	Function Generator (ScienTech, SM 5071, Sr.No.04051250,04091260,62) 3MHz	Scien Tech	3	29/9/2004	SE/IN/03-04/227	24024
11	Function Generator (ScienTech, ST 4061, Sr. No 0905875	Scien Tech	1	3/1/2006	RI/CS/05-06/247	7438
12	Audio Generator (AO-10)	Oswa	1			6975
13	CADDO 4061 10 MHz Function Gerator, 30 MHz Frequency Counter (1008770,778,784)	Scien Tech	3	4/11/2008	RI/IN/08-09/162	21656
14	Multiple Power Supply (ScienTech, ST 4074, Sr.No.0702145,)	Scien Tech	1	12/10/2002	1605	9900
15	Triple Power Supply (ScienTech, ST 4071Sr.No.0802235)	Scien Tech	1	12/10/2002	1605	6200
16	Triple Power Supply (ScienTech, ST 4071Sr.No.0704555)	Scien Tech	1	29/9/2004	SE/IN/03-04/227	5236
17	Dual Power Supply (Scientific, HM 5041, Sr.No. 0700152,0700151,)	Scien tific	2	3/8/2000	866	12300

18	Regulated Power Supply (Autonix)	Autonix	2	1/10/1999	609	3600
19	ST 4071 Tripple Power Supply (10081173,174,175)	Scien Tech	3	4/11/2008	RI/IN/08-09/163	17064
20	ST 4074 Multiple Power Supply (10081006,1009)	Scien Tech	2	4/11/2008	RI/IN/08-09/163	16626
21	Digital Multimeter (4022) Scientific	Scien tific	2	3/8/2000	866	4500
22	Digital Multimeter (DM 375) Motwane	Motwan	2	1/10/1999	609	4208
23	Analog Multimeter Sanwa	Sanwa	2	1/10/1999	609	600
24	Digital Multimeter (MAS 830, MasTech)	Mas Tech	2	19/1/2006	740	380
25	Two Stage RC coupled Amplifier Trainer Kit (ETB-45) (Sr. No. 65610, 11) OMEGA	Scien Tech	2	6/12/1999 10/12/99	8664 676	2600
26	Transistorized Hartley & Colpitts Oscillator Trainer Kit (OSAW)	Oswa	1	3/10/1999	613	3000
27	Zener Diode Characteristics Trainer Kit (INCO)	Inco	1	22/04/98	95	1700
28	FET characteristics Trainer Kit (ETB-53) (Sr.No. 65309, OMEGA)	Omega	2	6/12/1999 10/12/99	8664 676	9600
29	DMM demonstrator (OMEGA)	Omega	1	6/9/2000	908	3705
30	PN junction diode characteristics	Scien Tech	1	22/04/98	95	1700
31	PNP-NPN char(PISCO)	Pisco	1	22/04/98	95	2400
32	PNP-NPN char(INCO)	Inco	1	8/9/1998	338	2750
33	Hybrid Parameters of transistor	Omega	2	6/12/1999 10/12/99	8664 676	6400
34	MOSFET characterisics	Oswa	2			7150
35	Wideband Amplifier	Omega	2	6/12/1999 10/12/99	8664 676	3200
36	RC & LC Oscillators	Inca	1	3/10/1999	613	3600
37	Meter 100mA	Madan	5	16/9/2005	176	425
38	Meter 100microA	Madan	4	16/9/2005	176	420
39	Meter 30V	Madan	5	16/9/2005	176	225
40	Meter 300V	Madan	5	16/9/2005	176	175
41	Meter 1V	Madan	5	16/9/2005	176	425
42	Meter 20V	Madan	5	16/9/2005	176	425
<b>Total =</b>						<b>458401</b>

### ABOUT THE ELECTRONICS ENGINEERING LAB

#### Preamble:-

Electronics components are used everywhere in the industrial environment and in every electronic system appears as immense need to ensure functioning of the system according to designed outcomes. Different types of devices are used for different applications e.g. amplification of weak signals, switching circuits etc. Laboratory housed with basic apparatus required and basic components in adequate quantity and quality according to list of experiments. The laboratory explored with self explanatory charts mounted on wall chart boards. It is being updated with the chart prepared by students in lab. We assign an object to students for getting the desired output of the devices and circuits.

#### Pre-requisite:-

Effectiveness of the laboratory realize when effective theoretical knowledge is being provided, for this laboratory assigned in curriculum along with the subject in same semester that's why student gains sound theoretical knowledge when he/she comes in lab. We also ensure same by providing Pre-experiment questions.

#### Objective:-

1. Give the operation/working of basic apparatus e.g. CRO, Function Generator etc.
2. To perform rigorous experiments to consolidate basic knowledge in electronics engineering.
3. Provide a platform for students to practical implementation of Electronics Circuits and projects.